 


CSE 260 DIGITAL LOGIC DESIGN

Combinational Circuits- 1

Introduction

- Two classes of logic circuits:
 - ❖ combinational
 - ❖ sequential
- **Combinational Circuit:**



Combinational Circuit vs. Sequential Circuit




Combinational

- A combinational circuit consists of logic gates whose **outputs** at any time **are determined directly from the present combination of inputs** without regard to previous inputs.
- A combinational circuit **performs** a specific information-**processing** operation fully **specified** logically **by** a set **of Boolean functions**.

Sequential


- Sequential circuits employ memory elements in addition to logic gates. **Their outputs are a function of the inputs and the state of memory elements**
- The state of memory elements, in turn, is a function of previous inputs. As a consequence, the **outputs** of a sequential circuit **depend not only on present inputs, but also on past inputs**.

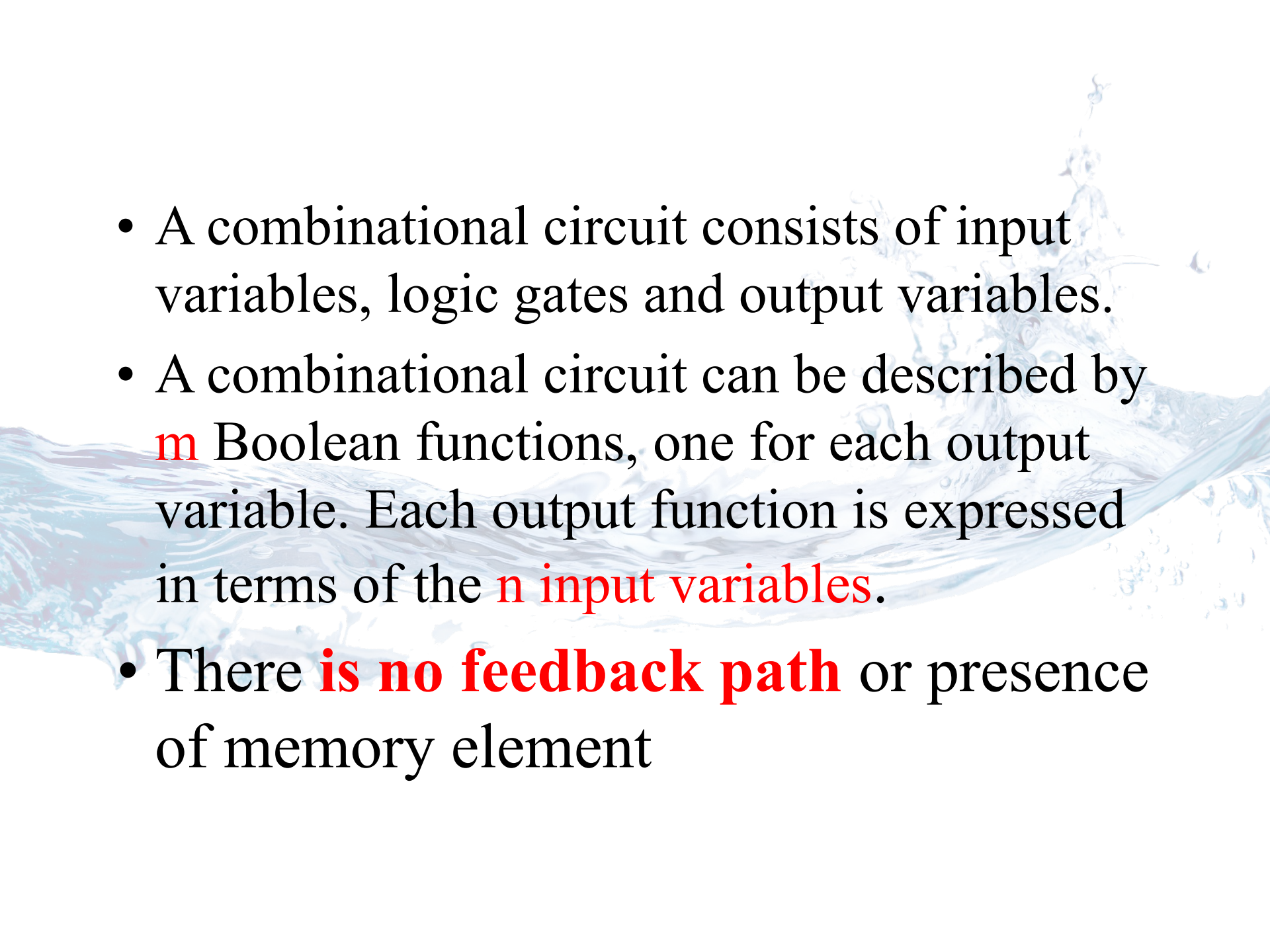- 
- A decorative background featuring a dynamic splash of water in shades of blue and white, creating a sense of movement and freshness.
- A combinational circuit consists of input variables, logic gates and output variables.
 - A combinational circuit can be described by **m** Boolean functions, one for each output variable. Each output function is expressed in terms of the **n input variables**.
 - There **is no feedback path** or presence of memory element

Design Procedure:

The design of combinational circuits starts from the verbal outline of the problem and ends in a logic circuit diagram.

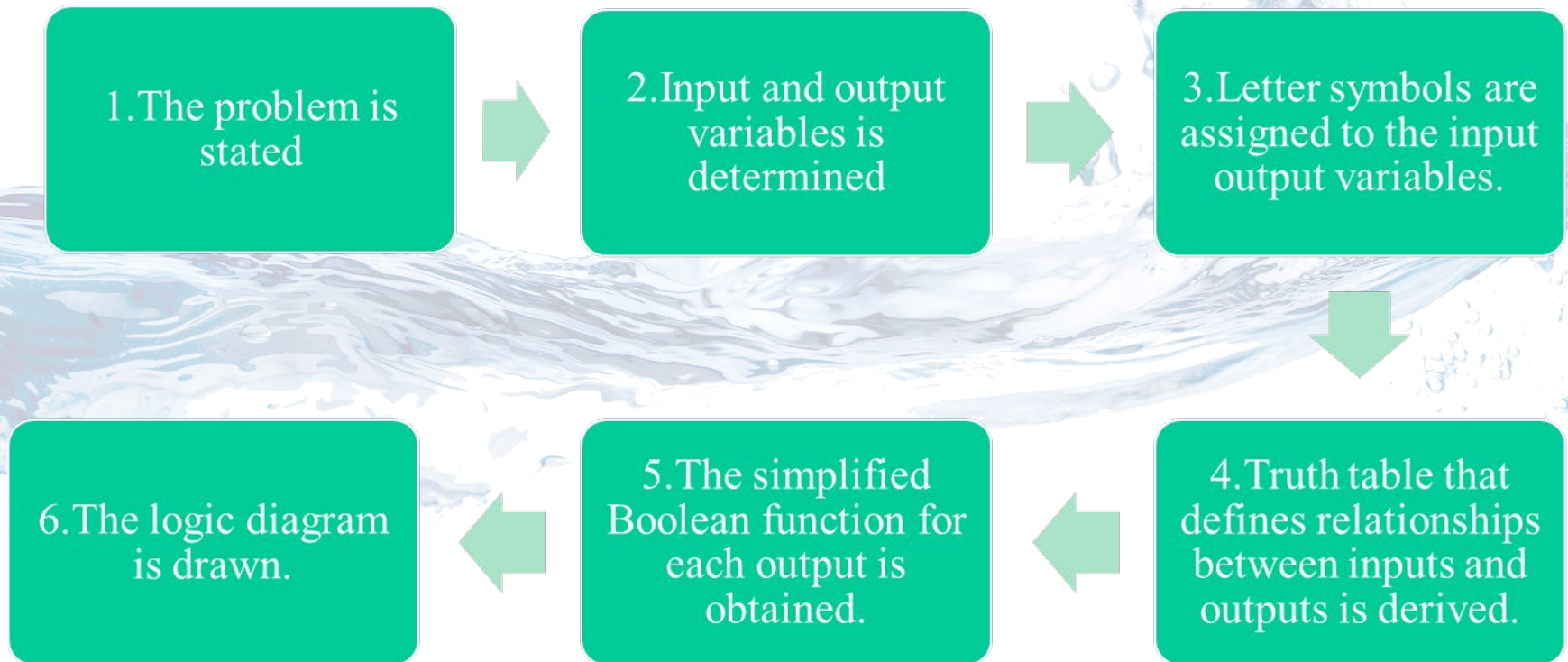
The procedure involves the following steps:



Hint: Aren't these the steps used for solving car-garage alarm system?!!!! So we are familiar with combinational circuit design! 😊

Design Procedure: Half Adder

 - The combinational circuit that performs the addition of two bits is called a half-adder.
- 1) State Problem
Example: Build a **Half Adder** to add two bits
- 2) Determine and label the inputs & outputs of circuit.
Example: Two inputs and two outputs labeled, as follows:



- 3) Draw truth table.

Design Procedure: Half Adder

4) Obtain simplified Boolean function.

Example: $C = XY$

$S = X'Y + XY' = X \oplus Y$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

5) Draw logic diagram.

Half Adder


Ways to draw half-adder

- Most commonly used

$$S = xy' + x'y$$

$$= x \oplus y$$

$$C = xy$$

 

(e) $S = x \oplus y$
 $C = xy$


Design Procedure : Full Adder

- Half-adder adds up only two bits.
- To add two binary numbers, we need to add 3 bits (including the *carry*).

■ Example:

	1	1	1		carry
	0	0	1	1	X
+	0	1	1	1	Y
	1	0	1	0	S

 - Need **Full Adder** (so called as it can be made from two half-adders).



Design Procedure : Full Adder

- Truth table:

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>s</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z - carry in (to the current position)

C - carry out (to the next position)

- From truth table

$$C = X'YZ + XY'Z + XYZ' + XYZ$$

$$S = X'Y'Z + XYZ + X'YZ' + XY'Z'$$

Gate-level (SSI) Design: Full Adder

Full Adders (3 bits)

$$\begin{aligned}C &= X'YZ + XY'Z + XYZ' + XYZ \\&= Z(X'Y + XY') + XY(Z + Z') \\&= Z(X \oplus Y) + XY\end{aligned}$$

$$\begin{aligned}S &= X'Y'Z + X'YZ' + XY'Z' + XYZ \\&= X'(Y'Z + YZ') + X(Y'Z' + YZ) \\&= X'(Y \oplus Z) + X(Y \oplus Z)' [(Y \oplus Z) = A] \\&= X'A + XA' \\&= X \oplus A \\&= X \oplus Y \oplus Z\end{aligned}$$


<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Gate-level (SSI) Design: Full Adder

- Circuit for above formulae:

$$C = XY + (X \oplus Y)Z$$

$$S = (X \oplus Y) \oplus Z$$

 

Full Adder made from two Half-Adders (+ OR gate).

Design Methods

- Different combinational circuit design methods:
 - ❖ Gate-level method (with logic gates)
 - ❖ Block-level design method
- Design methods make use of logic gates and useful functional blocks.
 - ❖ These are available as Integrated Circuit (IC) chips.

Why is it better to use IC than classical gate method?

- IC consists of gates all packed up together internally, which keeps the **gates safe inside** as well as makes it **economical by reducing external interconnection wires**
- As number of input increase, making the truth table and k-map gets cumbersome

Design Methods


- Type of IC chips (based on packing density) :
 - ❖ Small-scale integration (SSI): up to 12 gates
 - ❖ Medium-scale integration (MSI): 12-99 gates
 - ❖ Large-scale integration (LSI): 100-9999 gates
 - ❖ Very large-scale integration (VLSI): 10,000-99,999 gates
 - ❖ Ultra large-scale integration (ULSI): > 100,000 gates
- *Main objectives of circuit design:*
 - ❖ (i) reduce cost
 - reduce number of gates (for SSI circuits)
 - reduce IC packages (for complex circuits)
 - ❖ (ii) increase speed
 - ❖ (iii) design simplicity (reuse blocks where possible)

Block-Level Design Method

- More complex circuits can be built using block-level method.
- In general, block-level design method (as opposed to gate-level design) relies on algorithms or formulae of the circuit, which are obtained by **decomposing the main problem to sub-problems** recursively (until small enough to be directly solved by blocks of circuits).

4-bit Parallel Adder

 - Consider a circuit to add two 4-bit numbers together and a carry-in, to produce a 5-bit result:



- 5-bit result is sufficient because the largest result is:

$$(1111)_2 + (1111)_2 + (1)_2 = (11111)_2$$

4-bit Parallel Adder

- SSI design technique should not be used.
- Truth table for 9 inputs very big, i.e. $2^9=512$ entries:

$X_4X_3X_2X_1$	$Y_4Y_3Y_2Y_1$	C_1	C_5	$S_4S_3S_2S_1$
0 0 0 0	0 0 0 0	0	0	0 0 0 0
0 0 0 0	0 0 0 0	1	0	0 0 0 1
0 0 0 0	0 0 0 1	0	0	0 0 0 1
...
0 1 0 1	1 1 0 1	1	1	0 0 1 1
...
1 1 1 1	1 1 1 1	1	1	1 1 1 1

- Simplification very complicated as no. of input is 9 so $512(=2^9)$ possible combination will be there in truth table!

4-bit Parallel Adder

- Alternative design possible.
- Addition formula for each pair of bits (with carry in).

output

$$C_{i+1} S_i = X_i + Y_i + C_i$$

input

has the same function as a full adder.


$$C_{i+1} = X_i Y_i + (X_i \oplus Y_i) C_i$$

$$S_i = X_i \oplus Y_i \oplus C_i$$

NB: Similar to FA equation
 $C = XY + (X \oplus Y)Z$
 $S = (X \oplus Y) \oplus Z$

4-bit Parallel Adder

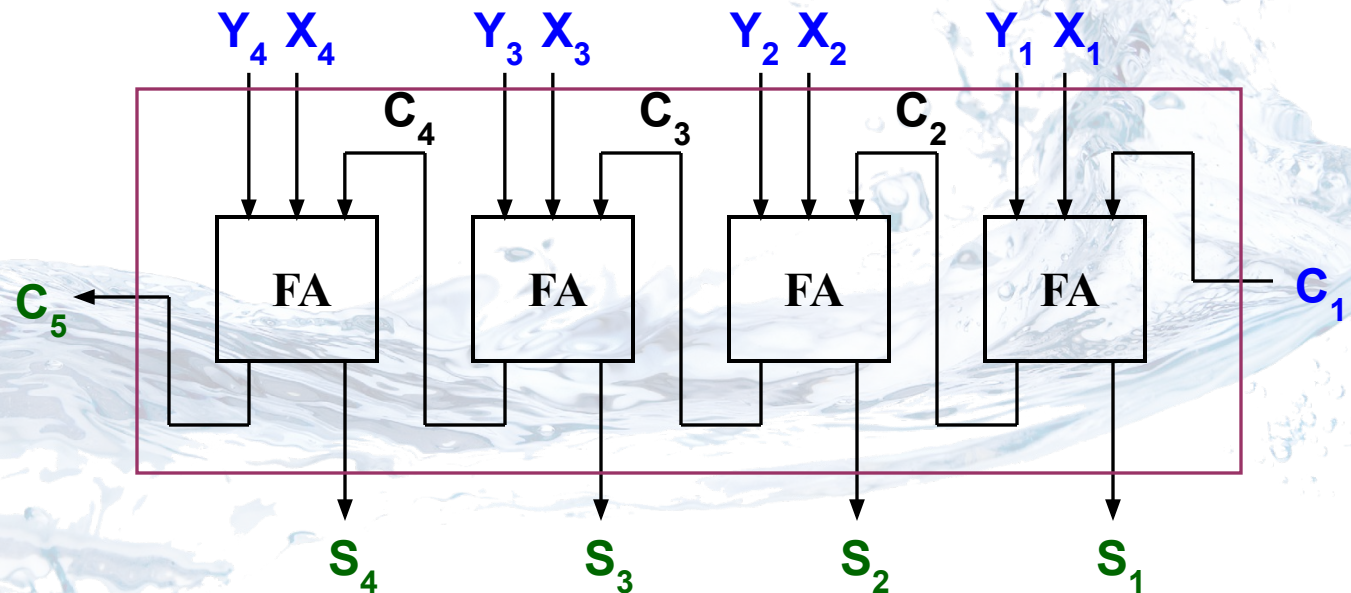- Cascading 4 full adders via their carries, we get:



■ Input
■ Output


n -bit full adder requires n full- adders

Examples

- Simple examples using 4-bit parallel adder as building blocks:
 - ❖ 16-Bit Parallel Adder
 - ❖ Adder cum Subtractor
 - ❖ BCD to excess 3 code converter

4-bit Parallel Adder-Subtractor

 - Subtraction can be performed through addition using 2s-complement numbers.
- Hence, we can design a circuit which can perform **both addition and subtraction**, using a parallel adder.



4-bit Parallel Adder-Subtractor

- The control signal $S=0$ means add
 $S=1$ means subtract

- Recall that:

$$X - Y = X + (-Y)$$

$$= X + (\text{2's complement of } Y)$$


$$= X + (\text{1's complement of } Y) + 1$$

$$X + Y = X + (Y)$$

4-bit Parallel Adder cum Subtractor

- Design requires:

(i) **XOR** gates:

 


such that: output = Y when S=0
= Y' when S=1

(ii) **S** connected to carry-in.

S	Y	Output
0	0	0
0	1	1
1	0	1
1	1	0

4-bit Parallel Adder cum Subtractor

- Adder cum subtractor circuit:

 

Analysis:


If $S=1$, then
 $X + (1\text{'s complement of } Y) + 1$
appears as the result.

If $S=0$, then $X+Y$ appears as
the result.

A 4-bit adder cum subtractor

16-bit Parallel Adder

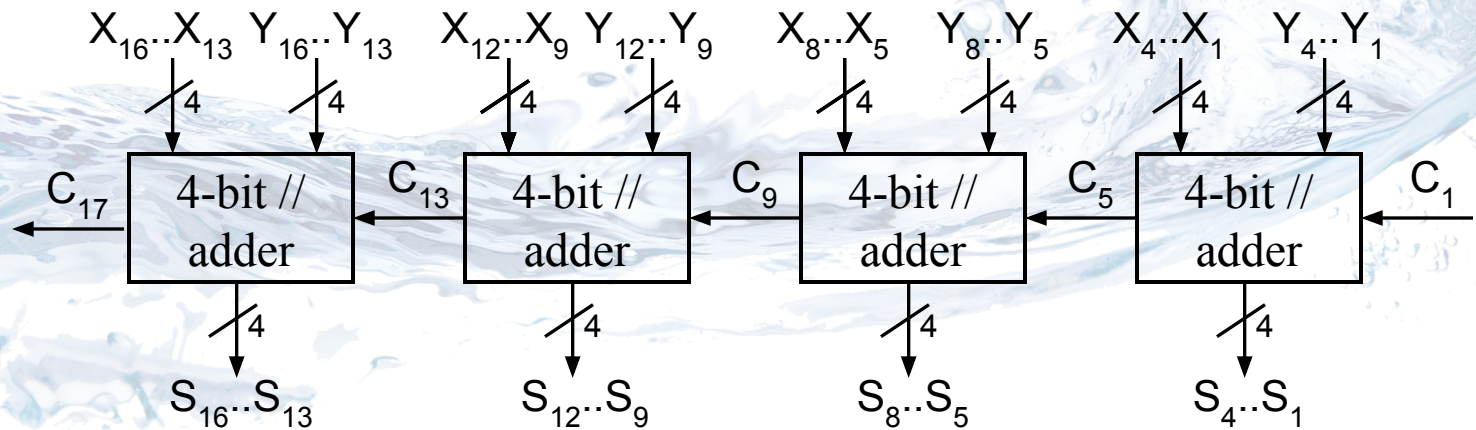
- Larger parallel adders can be built from smaller ones.
- Example: a **16-bit parallel adder** can be constructed from four 4-bit parallel adders:



A 16-bit parallel adder

16-bit Parallel Adder

- Shortened notation for multiple lines.

 


16-bit parallel adder ripples carry from one 4-bit block to the next.

Such ripple-carry circuits are “slow” because of long delays needed to propagate the carries.


Arithmetic Circuits: Cascading Adders

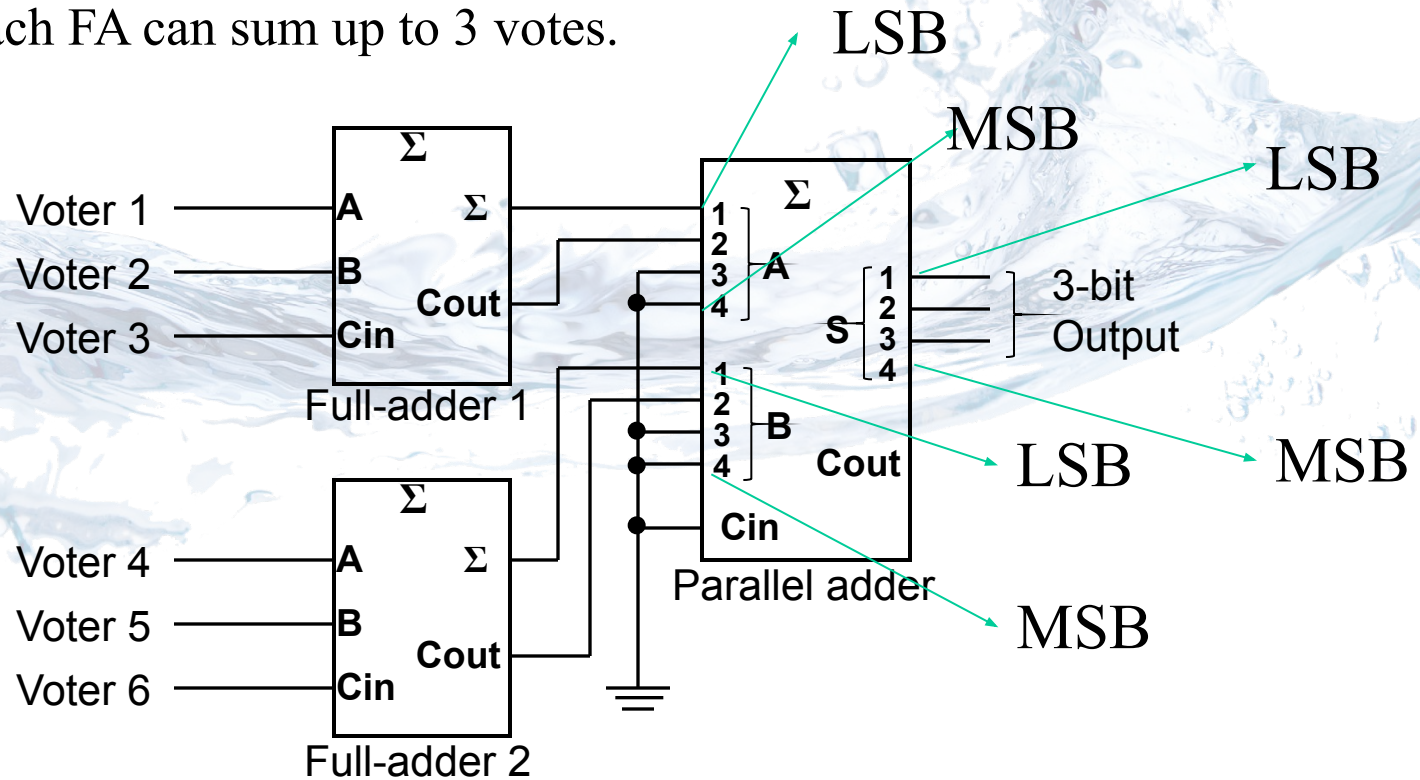- Application: 6-person voting system.
 - ❖ Use FAs and a 4-bit binary parallel adder.
 - ❖ Each FA can sum up to 3 votes.




Try it yourself

- Design a 12 person voting system

 


Solution

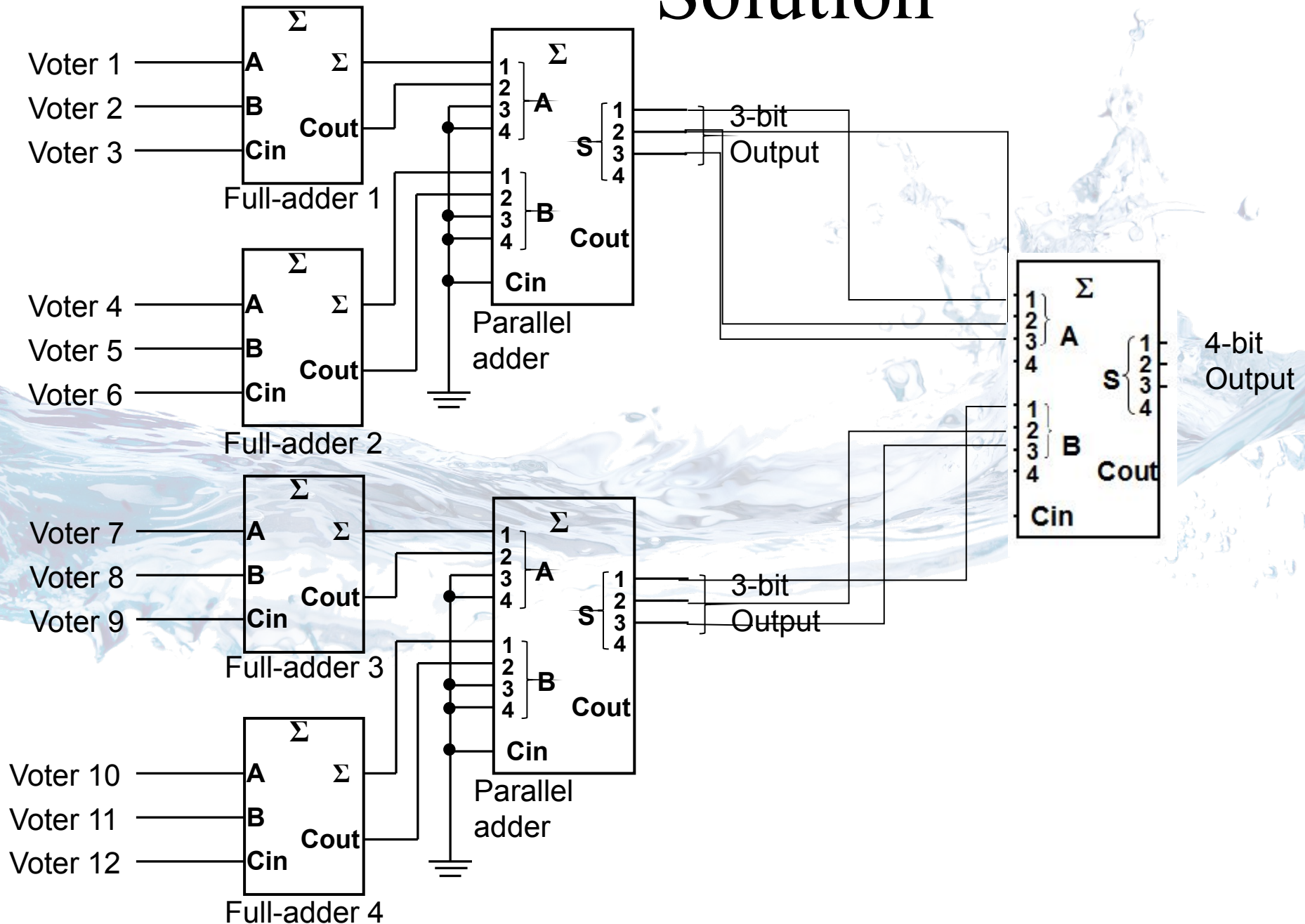


Try it yourself

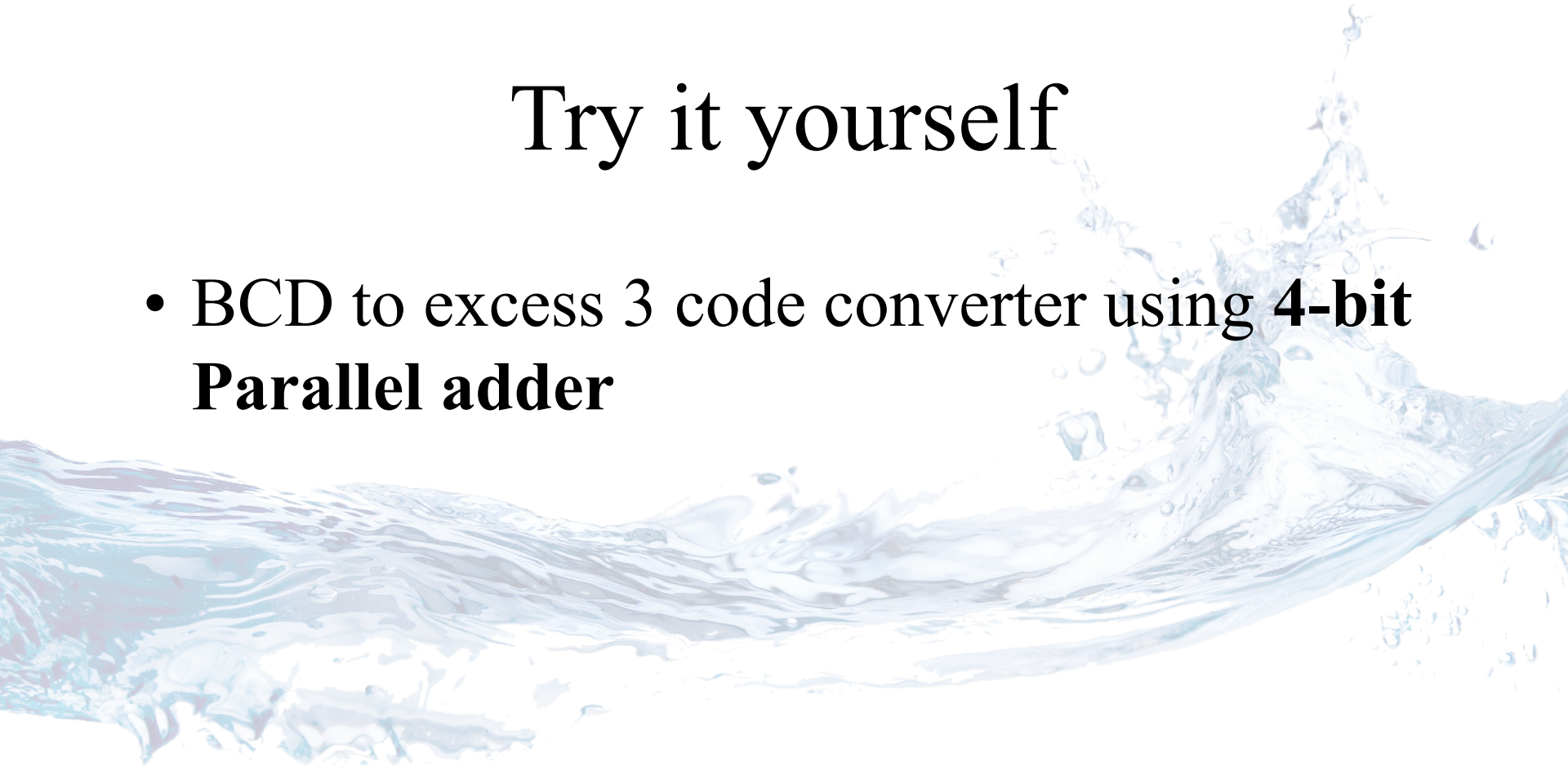- BCD to excess 3 code converter using **4-bit Parallel adder**




BCD to excess 3 code converter

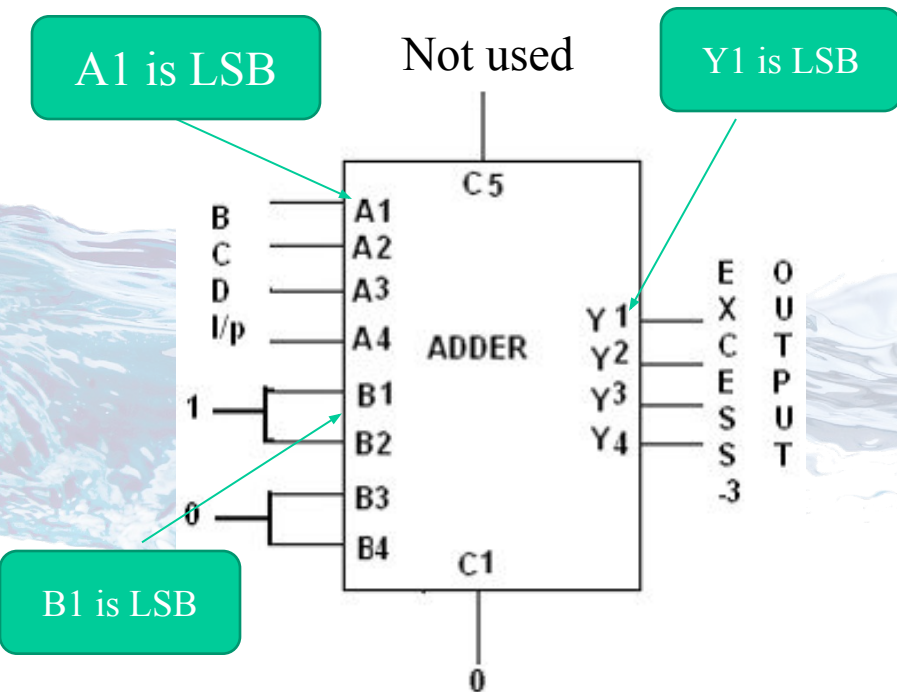

Inspection of truth table of 'excess 3 from bcd' shows that we can get excess-3 code from bcd by adding '0011' to each BCD number. This addition can be implemented by means of 4-bit full adder MSI circuit.

Code Converters

 - Code converters – take an input code, translate to its equivalent output code.



- Example: **BCD to Excess-3 Code Converter.**

Input: BCD digit

Output: Excess-3 digit