




CSE260 Digital Logic Design


# Karnaugh Maps
 
# The map method

- The map method provides a simple procedure for minimizing Boolean functions.
- The map is made up of squares where each square represents a minterm.
- We represent each minterm of an equation by '1's
- We group the adjacent '1's in groups of 2, groups of 4 or groups of 8 and so on.
- In those groupings try to find the common literal.
- The map method is often known as Karnaugh Map or Veitch Diagram. In short we will call it K-map



(a)

 



(b)

## K Map Grouping Rules :


- i) Group the adjacent '1's in groups of 2, 4, 8 and so on  $[2^n]$
- ii) Take maximum number of 1 if possible.
- iii) You can cover a 1 multiple times only if that covered '1' can help another uncovered '1' to get covered.
- iv) Our target is to group all the '1's
- v) In case of "don't care" we can consider 'X' to create groups alongside '1's. Other rules stay same as always.
- vi) However, you cannot create groups with 'X' only. 'X' can ~~be~~ only be used to create uncovered '1's. groups if it is helping any
  
# Two variable map

- There are 4 minterm of 2 variable; hence the map is four squares, one for each minterm.



(a)

 

(b)

# Representing function in K-map

(a)  $F1 = xy$ ;

		$y$	
		0	1
$x$	0		
	1		1

(a)  $xy$

(b)  $F2 = xy' + xy + x'y$

$$\begin{aligned} &= x(y' + y) + x'y \\ &= x + x'y \\ &= (x + x')(x + y) \\ &= (1)(x + y) \\ &= x + y \end{aligned}$$

		$y$	
		0	1
$x$	0		1
	1	1	1

(b)  $x + y$

# Try it yourself

$F = xy' + x'y' + x'y$ ,  
Simplify the equation using k-map

## Solution

- $F = xy' + x'y' + x'y = x' + y'$

		y	
		0	1
x	0	1	1
	1	1	

# Three variable map

- Sequence in 3-variable map is not in binary sequence but in reflected code. In reflected code, at a time only 1 bit changes from 0 to 1 and 1 to 0.
- Numbering of minterms follow binary numbers. Example  $m_5$  is at 101 i.e. row 1 and column 01.

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$



		yz			
		00	01	11	10
x	0	000	001	011	010
	1	100	101	111	110

Note: Any 2 adjacent square differ by 1 variable ( which is primed in one and unprimed in the other )

		yz			
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$

and unprimed in the other ) and they are grouped, then any 2 minterms in the adjacent square are ORed, will remove the different term. As a result , we get a single ANDed term of only 2 common literals

  
- $F1 = \sum(5,7) = xy'z + xyz = xz(y' + y) = xz$
- $F2 = \sum(0,2) = x'y'z' + x'yz' = x'z'(y' + y) = x'z'$




 
# Simplifying functions using k-map


- $F = \sum(2,3,4,5) = x'yz + x'yz' + xy'z' + xy'z$   
 (note: in other words,  $F = (\sum (010, 011, 100, 101))$  so place 1's in these positions and group the 1's)  
 $F = x'y + xy'$



- Grouping of 1 can be done in groups of two '1', four '1', eight '1'.... $2^n$  '1'.


■  $F1 = x'yz + xy'z' + xyz + xyz' = xz' + yz$

011      100      111      110

 

Notice even 2 opposite edges of the map are adjacent, thus they can be grouped

 - If  $F = \sum(0, 2, 4, 6)$ , then simplify it




$$\begin{aligned}
 m_0 + m_2 + m_4 + m_6 &= x'y'z' + x'yz' + xy'z' + xyz' \\
 &= x'z'(y' + y) + xz'(y' + y) \\
 &= x'z' + xz' = z'(x' + x) = z'
 \end{aligned}$$

# Try it yourself

- $F = \sum(0, 2, 4, 5, 6)$ , Simplify it.

## Solution

 

[ Try it yourself: ]

- $F = A'C + A'B + AB'C + BC$ 
  - a) Express it as SOP (i.e.  $\Sigma$ )
  - b) Simplify it using Kmap

# Solution

■ (a)  $F = \sum(1, 2, 3, 5, 7)$

(b)  $F = C + A'B$

	$BC$	00	01	11	10
$A$	0		1	1	1
1			1	1	

To find  $A'C$ , coincide  $A'$  (first row) with  $C$  (middle 2 column)

To find  $A'B$ , coincide  $A'$  (first row) with  $B$  (last 2 column)

To find  $BC$ , coincide  $B$  (last 2 column) with  $C$  (middle 2 column)

To find  $AB'C$ , is m5( 2<sup>nd</sup> row 2<sup>nd</sup> column)

# Summary of grouping in 3-variable map

One square represents one minterm, giving a term of three literals.

Two adjacent squares represent a term of two literals.

Four adjacent squares represent a term of one literal.

Eight adjacent squares encompass the entire map and produce a function that is always equal to 1.

		yz			
		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$

# Four variable map

- Adjacent squares can be side by side or lie in 4 corner or top-bottom or left-right edge condition. Example,  $m_0$  -  $m_2$  are adjacent and similarly  $m_3$  -  $m_{11}$  are adjacent

One square represents one minterm, giving a term of four literals.  
 Two adjacent squares represent a term of three literals.  
 Four adjacent squares represent a term of two literals.  
 Eight adjacent squares represent a term of one literal.  
 Sixteen adjacent squares represent the function equal to 1.

		yz		y	
		00	01	11	10
wx	00	0000	0001	0011	0010
	01	0100	0101	0111	0110
11	11	1100	1101	1111	1110
	10	1000	1001	1011	1010

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)


		yz		y	
		00	01	11	10
wx	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
11	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$

(b)



- Simplify  $F = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
- Note: it is allowed to use the same '1' more than once.

wx \ yz	00	01	11	10
00	1	1		1
01	1	1		1
11	1	1		1
10	1	1		

 

Try it yourself

■  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$


AB	CD		C	
	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

*A* { *B* { *D*

# [ Solution ]

■  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$

$F = B'D' + B'C' + A'CD'$


 


# [ Don't Care condition ]

- Don't cares in a Karnaugh map, or truth table, may be either **1**s or **0**s, as long as we don't care what the output is for an input condition we never expect to see.
- We plot these cells with a special sign, 'X', among the normal **1**s and **0**s.
- When forming groups of cells, treat the don't care cell as either a **1** or a **0**, or ignore the don't cares. This is helpful if it allows us to form a larger group than would otherwise be possible without the don't cares.
- There is no requirement to group all or any of the don't cares. (i.e. do not make any group only consisting the don't cares). Only use them in a group if it simplifies the logic.

Simplify  $F(w,x,y,z) = \sum(1,3,7,11,15)$  and don't care  $d(w,x,y,z) = \sum(0,2,5)$

  Solution: Even though 2 solutions are not same, but either 1 is acceptable. Such scenario only applicable for Don't care scenarios!



# **APPLICATIONS OF K-MAP**

# Example 1: Design and draw the circuit diagram of BCD to Excess-3 code converter

BCD Input				Excess-3 Output			
B3	B2	B1	B0	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

Q1. Treat each W, X, Y and Z as a function and write them as SOP

W X  
Y Z

Q2. Based on the SOP, draw the circuit diagram of BCD to Excess-3 code converter


Any value higher than 9 will result into don't care output

For W

AB \ CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$W = A + BC + BD$$

$$= A + B(C + D)$$

 

For X

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$X = B\bar{C}\bar{D} + \bar{B}(C + D)$$

For Z

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1			X

$$Z = \bar{D}$$

For Y


AB \ CD	00	01	11	10
00	1		1	
01	1		1	
11	X		X	X
10	1		X	X

$$Y = \bar{C}\bar{D} + CD$$



# Example 2: 7 segment display board

Display digit	b8	b4	b2	b1	A	B	C	D	E	F	G
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
off	1	0	1	0	×	×	×	×	×	×	×
off	1	0	1	1	×	×	×	×	×	×	×
off	1	1	0	0	×	×	×	×	×	×	×
off	1	1	0	1	×	×	×	×	×	×	×
off	1	1	1	0	×	×	×	×	×	×	×
off	1	1	1	1	×	×	×	×	×	×	×

 

Segment a

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	1	1	
!A	B	0	1	1	0	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + CD + B D + !B !D$$

Segment b

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	1	1	1	
!A	B	1	0	1	0	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$!B + !C !D + C D$$

Segment c

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	1	1	0	
!A	B	1	1	1	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$B + !C + D$$

Segment d

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	1	1	
!A	B	0	1	0	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + C !D + !B !D + !B C + B !C D$$

Segment e

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	0	1	
!A	B	0	0	0	1	
A	B	D	D	D	D	
A	!B	1	0	D	D	

$$C !D + !B !D$$

Segment f

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	0	0	
!A	B	1	1	0	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + B !C + !C !D + B !D$$

Segment g

			!C	!C	C	C
			!D	D	D	!D
!A	!B	0	0	1	1	
!A	B	1	1	0	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + B !C + B !D + !B C$$

# [ Try it by your self ]

- A **car garage** has a front door and one window, each of which has a sensor to detect whether it is open. A third sensor detects whether it is dark outside. A security system for the garage follows this rule: the alarm rings if the **alarm switch is turned on** and **either the front door is not closed or it is dark and the side window is not closed**.

# [Solution]

Switch On	Door	Window	Dark	AlarmRing
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

WDk

SDr

		1	1
		1	

$$\text{AlarmRing} = \text{SWDk} + \text{SDrW}$$

Assuming

**AlarmRing** = 1 if Alarm rings, 0 otherwise.

**Switch On** = 1 if alarm switch is on, 0 otherwise


**Door** = 1 if door is not closed, 0 otherwise.

**Window** = 1 if window is not closed.

**Dark** = 1 if it is dark outside, 0 otherwise.

# [Solution

Switch On	Door	Window	Dark	AlarmRing
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

 

$$\text{AlarmRing} = \text{SWDr} + \text{SDrW}$$

## Next Step

- You do have to draw the circuit for the above function
- You may be asked to draw the circuit using basic gates or universal gates
- By now, you should be able to do it yourself. So please try.